RED 37.75

5300 slits/cm

BLUE 27 OR 29.5

VIOLET 23.5

~~L = 5 cm~~

$\sin\theta = \frac{x}{\sqrt{x^2+y^2}}$ or $\tan\theta = \frac{1.5}{100}$

$\lambda = d \sin\theta$

Alex Goyette

(11) FRICTION IS A FORCE OF RESISTANCE i.e. it is subtracted from the actual force to get the resultant. Force is measured in N.

(13) Friction is subtracted from the actual force, to get the result. If friction ~~is decreased~~ ~~increases~~ exists in a machine, the result will be smaller, therefore decreasing efficiency.

WINDOW PAIN
1 DC
0 COMP
PIZZA

$\frac{\text{JOULE}}{\text{COULOMB}} = \text{VOLT}$

$P = iV \quad P = V^2/R \quad P = i^2R$ from OHM'S LAW $i = V/R \quad V = iR \quad R = V/i$

$Q_{CAL} = (.24 \frac{\text{CAL}}{\text{JOULE}})(P_{\text{WATTS}})(t_{\text{SECONDS}})$ kilowatthour $= P \cdot t$

.24 CAL/JOULE

RED + BLK −

$R = \rho \frac{L}{A}$ (wire resistance)

ρ of R R_1 R_2 R_3 add $\rho\frac{L_1}{A} + \rho\frac{L_2}{A}$ ρ/A (−)

SERIES

$R_T = R_1 + R_2 \ldots$
$I_T = I_1 = I_2 \ldots \quad I_1 = I_2$ CURRENT ALWAYS SAME
$V_T = V_1 + V_2 \ldots$
$P_T = P_1 + P_2 \ldots$

fuse ∿ fusable link

bimaterial metal ∿ circuit breaker — top metal heats + bends more

$G = \frac{1}{R}$ conductance (mhos) ∿

Rheostat ∿ variable resistor ∿ moveable connector

Ammeter goes in series w/ resistor $R \approx 0$.
Voltmeter in parallel w/ supply or resistor, $R \approx \infty$

potentiometer

PARALLEL

$\frac{I}{\text{WATT-V}}$

$E_T = V_T = V_1 = V_2 = V_3$
$I_T = I_1 + I_2 + I_3 \ldots$
$\frac{E_T}{R_T} = \frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3}$
$\frac{I_T}{E_T} = \frac{I_1}{V_1} + \frac{I_2}{V_2} + \frac{I_3}{V_3}$
$G_T = G_1 + G_2 + G_3$
$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
$P_T = P_1 + P_2 + P_3$

Pd $\frac{1}{R}$ $\frac{E_T}{I_T}$ V_1 V_2 I_1 I_2 $\frac{V_T}{I_T}$ $\frac{V_1}{I_1}$ $\frac{V_2}{I_2}$
R_T R_1 $I_2 \ldots$

Two R's $\frac{I_1}{I_2} \quad \frac{R_2}{R_1}$
$R_T = \frac{R_2}{R_1 + R_2}$

20 75

4/08

G-AC GEN

curve for inductor's magnetism

E(I-E) 1° Lenz's law again! BACK emf

ON/OFF

mag field moves to be established

Transformer 2°

2° SOFT IRON CORE 1°

SWITCH

10 2°

use Pulse DC or AC to get AC

trim DC shorts out

$\frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{i_s}{i_p}$ $P_s = P_p$

CIRCUIT BREAKER

IRON

EMF = Blv

mag wire velocity

CV SP SHAPE

use capacitor to stop sparks

arev. $\frac{q}{V} = \frac{q}{kV}$

E = flow of photons

REcharge uses Xformer (lower volt) + RECTIFIER ( )

2 mini fonus otter - supposed material thru which light vibrates - wave

UV RAYS

energy of ejected electron

KEmax

fo freq (eV)

threshold position

much like collision

$\frac{\Delta KE}{\Delta F}$ = slope = h Planck's constant 6.6×10^{-34} J sec

$KE_{max} = hf - hf_o$

binding energy = work function

"You go from dis place to dis place it's displacement"

"The word falls includes the word did-not-throw-it-downward."

electrons

nodes = nodal point

electron as wave

momentum

$\lambda_{particle} = \frac{h}{mv}$ electrons are standing waves

for electron, λ = Angstrom - diam of atom

$F\Delta T = M\Delta V$ impulse = momentum

* The character-receive subroutine should be called with a parameter specifying the number of seconds to wait. The receiver should first call it with a time of 10, then <nak> and try again, 10 times.

After receiving the <soh>, the receiver should call the character receive subroutine with a 1-second timeout, for the remainder of the message and the <cksum>. Since they are sent as a continuous stream, timing out of this implies a serious like glitch that caused, say, 127 characters to be seen instead of 128.

* When the receiver wishes to <nak>, it should call a "PURGE" subroutine, to wait for the line to clear. Recall the sender tosses any characters in its UART buffer immediately upon completing sending a block, to ensure no glitches were mis-interpreted.

The most common technique is for "PURGE" to call the character receive subroutine, specifying a 1-second timeout, and looping back to PURGE until a timeout occurs. The <nak> is then sent, ensuring the other end will see it.

* You may wish to add code recommended by Jonh Mahr to your character receive routine - to set an error flag if the UART shows framing error, or overrun. This will help catch a few more glitches - the most common of which is a hit in the high bits of the byte in two consecutive bytes. The <cksum> comes out OK since counting in 1-byte produces the same result of adding 80H + 80H as with adding 00H + 00H.

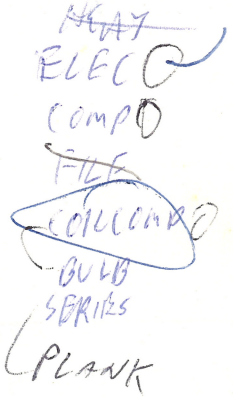

COMPASS

IRON FILE
COMPASS COIL
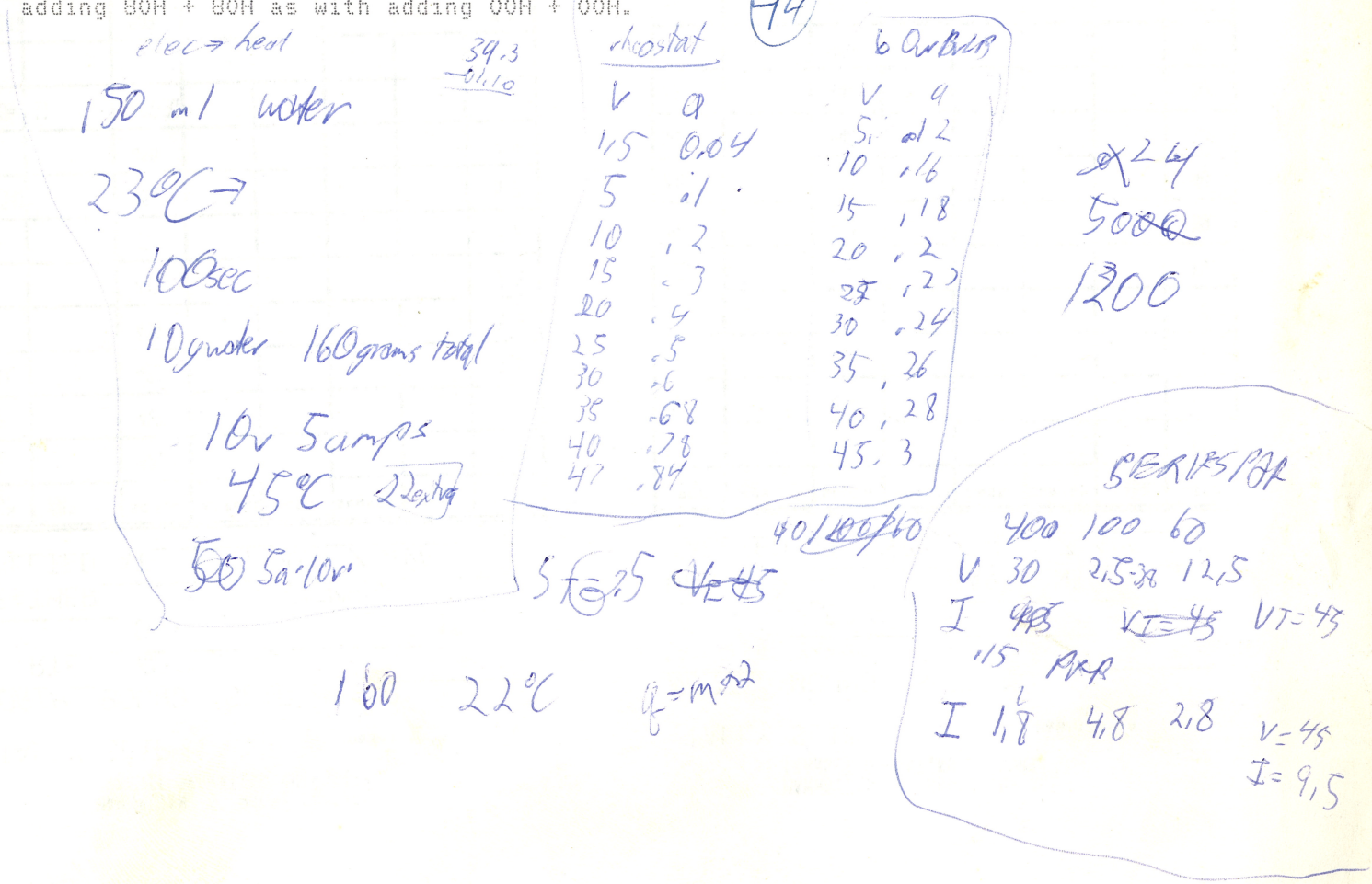
COMP
PLANK